



Figure 3

Based on National Semiconductor's LM5010, this buck-boost regulator operates over a wide input-voltage range.