



Figure 3

National Semiconductor's LM317 builds a precision current source for Cree's Xlamp demo board.