



Figure 4

A two-stage limiter can increase the achievable isolation beyond what one-stage version; the capacitor, Schottky diode, and directional coupler further lower the threshold of the circuit.