



Figure A

A clipping circuit (a) is similar in some ways to a limiter, but it uses antiparallel diodes and has a different transfer function (b).