



**Figure 2** The system wiring diagram shows transformer T<sub>1</sub>'s primary winding. Low-voltage-disconnect units LVD<sub>1</sub> and LVD<sub>2</sub> isolate the 48V battery or the customer's load for maintenance.