



**Figure 1**

In this circuit, the LED driver drives the 4- to 20-mA current loop proportionate to a sensed temperature of  $-10^\circ\text{C}$  at 4 mA and  $50^\circ\text{C}$  at 20 mA.