



**Figure 2** A laser-diode simulator requires only one transistor.