



Figure 2

This oscilloscope photo shows circuit's internal waveforms:

Trace 1 is the integrator's output voltage, Trace 2 is the comparator's output voltage, Trace 3 is the inverter's output voltage, and Trace 4 is the PPM-output voltage.