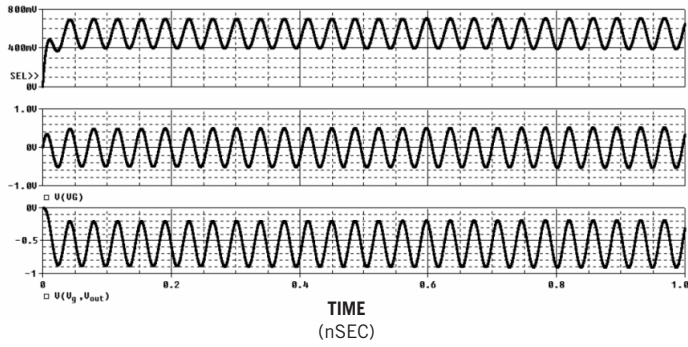


$V_{OUT}$   
(V)

**Figure 4**



With  $C_1$  having a value of 50 nF and  $C_2$  having a value of 114 nF, the circuit oscillates.