



Figure 1

Four 2.5V references, IC₁ through IC₄, produce 10V. Resistors R₁ and R₂ form a voltage divider that reduces the 10V output to 2.5V and lowers the output-noise voltage by half. Buffer amplifier IC₅ isolates the reference circuit from the load.