



Figure 1

Using MOSFETs and a relay, this electronic load can operate in both current- and voltage-regulation modes.