



**Figure 2**

You can use this RLC-resonant circuit to measure the modeled inductance in PSpice, using an ac sweep analysis.