



Figure 1

A conventional active voltage divider requires two op amps, IC₁ and IC₂, and two resistors, R₁ and R₂, that form a 2-to-1 voltage divider.