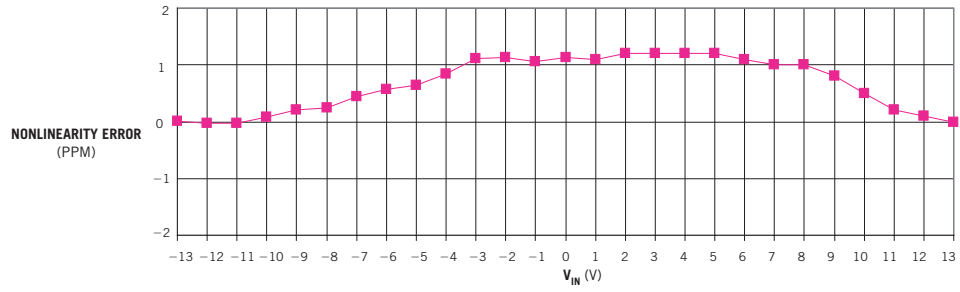


Figure 4



The circuit in Figure 2 introduces a maximum nonlinearity error of about 1 ppm over a 26V input-voltage range.