



Figure 1

Two ICs form a pulse-width-modulated keypad interface that uses only one microcontroller-input pin.