



Figure 1

Under control of its host processor, digital potentiometer IC₂ adjusts the processor's core power-supply voltage.