



(a)

(b)

Figure 1

To measure high voltages, you can use discrete resistors to assemble an input voltage divider and buffer (a) or an attenuating inverter (b), but performance suffers due to thermal mismatch.

performance suffers due to thermal mismatch.