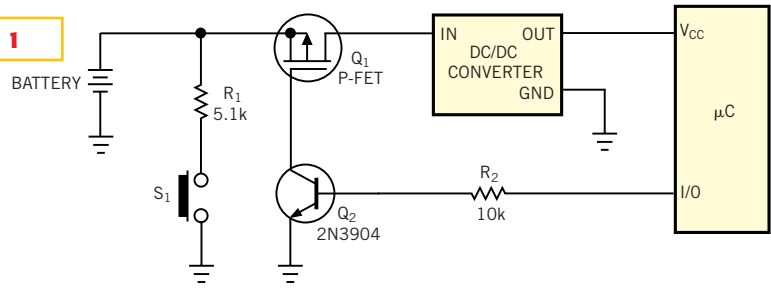


**Figure 1**



**This on/off circuitry is effective but can suffer from turn-on ambiguity.**