



Figure 2

Oscilloscope measurements of the VFC show voltage across capacitor C_5 (upper trace) and comparator IC_2 's output voltage, V_{OUT} (lower trace), for a nominal input voltage of 12V.