



**Figure 1**

This switched-capacitor inverter derives  $-10\text{V}$  from  $5\text{V}$ .