



**Figure 2**

At light loads, the circuit in Figure 1 delivers more than  $-10\text{V}$ ; at higher currents, the magnitude of the negative output voltage exceeds its positive input voltage of  $5\text{V}$ .