



Figure 1 A power-MOSFET-limiting circuit restricts inrush current and protects against output short circuits.