



Figure 1 Build a sine-wave source around a single high-speed CMOS hex inverter and a handful of components.