



Figure 1 Two ICs and two MOSFETs form the heart of this high-efficiency, wide-range voltage regulator.