



Figure 1 A basic switch-contact debouncer consists of an RC network followed by a Schmitt-trigger circuit.