



Figure 2 Adding watchdog protection to the circuit of Figure 1 guards against battery damage when the baseband processor stalls or ceases software execution.