



Figure 1 Based on the "barefoot" TPS61040, this dc/dc boost converter delivers output voltages only within IC_1 's ratings.