



Figure 2 Adding an external cascode-connected MOSFET transistor, Q_2 , with higher breakdown-voltage ratings, enables the circuit to produce higher output voltages.