



Figure 1 An added resistor, R_1 , helps improve light-load operation of a popular switched-mode power-supply controller by eliminating output asymmetry.