



Figure 1 Despite the block diagram, the TL431 is internally complex (a), but you need only three external resistors to use the TL431 in a basic shunt-regulator circuit (b).