



Figure 2 A TL431 replaces a more expensive operational amplifier in this power supply's PWM feedback-regulator circuit.