



**Figure 2** Adding two components,  $R_6$  and  $C_4$ , helps reduce output-ripple voltage and improve output-voltage regulation.