



Figure 1 A typical analog moving-coil voltmeter employs a high-value series resistor, R_S , to establish the full-scale range but doesn't contribute to electromagnetic damping of the meter movement.