



Figure 2 An operational amplifier's low output resistance provides electro-mechanical damping for a moving-coil meter for stable readings and enhanced resistance to mechanical shock and vibration. Connect V_{CC} to either an external power supply or the circuit's input terminal if V_{IN} exceeds IC_1 's minimum power-supply-voltage rating.