



Figure 3 Based on rail-to-rail operational amplifier IC₁, this circuit's input stage forms a diodeless, precision full-wave rectifier and enables the circuit of Figure 2 to display ac- or dc-voltage measurements on a dc meter.