



Figure 2 A zener-diode and resistor-voltage divider exhibits sensitivity to supply-voltage variations and allows LED brightness to vary.