



Figure 1 A thermistor-resistor network provides temperature compensation for a dc/dc converter's current-limit input, I_{LIM} .