



Figure 4 A NAND gate locks out trigger pulses, forming a nonretriggerable, monostable circuit.