



Figure 3 Because the two-phase converter's input-ripple currents are in phase opposition, the total input-ripple current is smaller than that of either phase.
