



Figure 4 In the single-phase converter, the output-filter capacitor supplies all of the output current during the FET's on-time. During the off-time, however, a current of $I_{OUT} \times d / (1 - d)$, or 14A, flows into the capacitor to recharge it.
