



Figure 7 This single-phase-boost converter uses only two ICs, one FET, and one inductor, but it includes 13 large aluminum-electrolytic capacitors.