



Figure 1 A parallel LC circuit and an amplifying voltage-to-current converter form a basic oscillator.