



Figure 3 In this improved design, pulse-width-controller IC_1 derives its power from R_T for start-up, auxiliary winding W_{AUX} for normal operation, and shunt-regulator circuit IC_2 and Q_1 for low-load operation.