



Figure 1 This simple circuit linearizes a thermistor's response and produces an output period that's proportional to temperature.