



Figure 2 Waveforms show input to comparator IC_2 (lower trace) and its output (upper trace). In the lower trace, IR_2 represents the voltage across R_2 .