



Figure 1 For low values of power-supply voltage, 2.8V maximum, use an analog switch at IC<sub>2</sub> that handles signal amplitudes to  $V_{DD} - 5.5V$  to direct IC<sub>1</sub>'s bipolar outputs to the headphone loads.