



Figure 2 Higher values of V_{DD} , 2.8 to 5.5V, require a different amplifier and a dual-supply-voltage switch at IC₂.