



Figure 3 When using a hands-free microphone/earphone kit as an alternative to stereo headphones, add the circuitry shown to avoid loading the microphone's output with the headphone-driver amplifier's output.