



Figure 1 The textbook complementary-CMOS pair (a) produces a clean output waveform with fast on/off transitions (b).