



Figure 1 You can assemble a bit-error-rate-measurement circuit from only a few components.